



# Chapter 20 Summary

## Essential Concepts and Formulas

# Electromotive Force and Current

- ◆ The maximum potential difference  $V$  is called the electromotive force ***emf*** (not not a force as the name implies)
- ◆ Flow of charge is called electric current,  $I$
- ◆ Measured in  $C/s =$  Ampere
- ◆ 2 Types of currents: Direct (DC) and Alternating (AC)

$$I = \frac{Vq}{Vt}$$

$$A = \frac{C}{s}$$

$$\xi = emf$$

# Ohm's Law

- ◆ Analagous to water flowing in a hose.
- ◆ In water, great pressure means larger water flow
- ◆ In electricity, greater voltage means larger current
- ◆ R=resistance
- ◆ Resistor: device that offers resistance
- ◆ Used to control current and voltage levels

$$V = IR$$

$$\frac{V}{I} = R$$

$$\frac{\text{volt}}{\text{ampere}} = \text{ohm}(\Omega)$$

# Resistance and Resistivity

- ◆ Like in a hose, resistance relates to length and area
- ◆ Rho is proportionality constant known as resistivity of material
- ◆ Rho is inherent property of material, like density
- ◆ Like density, changes with temperature

$$R = \rho \frac{L}{A}$$

# Electric Power

- ◆ Definition: When charge flows from A to B in a circuit, leading to current  $I$  and voltage  $V$ , the electric power is  $P=IV$
- ◆ Unit: Watt (W)
- ◆ Substituting other expressions for  $I$  and  $V$ , we obtain equivalent expressions for power

$$P = \frac{V_{\text{Work}}}{V_{\text{Time}}}$$

$$P = \frac{(Vq)V}{Vt} = \frac{Vq}{Vt} V = IV$$

$$P = IV$$

$$P = I(IR) = I^2 R$$

$$P = \left(\frac{V}{R}\right)V = \frac{V^2}{R}$$

# Alternating Current

- ◆ Similar to DC current, but voltage and current oscillate
- ◆ Equations are basically analogous to dc equations
- ◆ rms=root mean square. Obtained by dividing peak value by sqrt(2)
- ◆ Eqns aren't as important as concept of oscillation

$$V = V_0 \sin 2\pi ft$$

$$I = \frac{V_0}{R} \sin 2\pi ft = I_0 \sin 2\pi ft$$

$$P = I_0 V_0 \sin^2 2\pi ft$$

$$\bar{P} = \frac{1}{2} I_0 V_0 = \left(\frac{I_0}{\sqrt{2}}\right) \left(\frac{V_0}{\sqrt{2}}\right) = I_{rms} V_{rms}$$

$$\bar{P} = I_{rms} V_{rms}$$

$$\bar{P} = I_{rms}^2 R$$

$$\bar{P} = \frac{V_{rms}^2}{R}$$

# Series Wiring

- ◆ If devices are in series, the **current** is the same everywhere in the circuit
- ◆ Equivalent resistance is sum of individual resistors ( $R_s > R_n$ )
- ◆ You can still find power delivered to the resistors.
- ◆ In general, total power delivered is equal to power delivered to equivalent resistance

$$R_s = \sum R_n$$

$$V = IR_s$$

# Parallel Wiring

- ◆ If devices are in parallel, the **voltage** is the same across each branch
- ◆ Equivalent Resistance  
 $R_p < R_n$
- ◆ In general, total power is equal to power delivered to equivalent resistor
- ◆ Smallest resistance has largest impact (if one equals 0, short out occurs)

$$\frac{1}{R_p} = \sum \frac{1}{R_n}$$

$$I = V \frac{1}{R_p}$$



# Circuits Wired Partially in Both

- ◆ Strategy: Break it up into series/parallel parts
- ◆ Deal with isolated resistors, find equivalent resistance
- ◆ Slowly, keep adding one more part at a time, so slowly eliminating resistors
- ◆ Once again, easiest way is to break the circuit into manageable parts

# Internal Resistance and Kirchhoff's Rule

- ◆ Internal resistance: resistance of the battery depends on the current; the terminal voltage (delivered to the circuit) is the emf of the battery minus the internal resistance
- ◆ Junction rule: Current into a junction equals current out of a junction (conservation of charge)
- ◆ Loop Rule: For a closed-circuit loop, the total of all the potential drops is the same as the total of all the potential rises (conservation of energy)

# Measurement of Current and Voltage

- ◆ Ammeter: Measures current at some point in the circuit. Probes must be inserted in **series** with the circuit. Meter should have a negligible resistance.
- ◆ Voltmeter: Measures the voltage between two points. Probes must be inserted in **parallel** with the circuit. Meter should have a negligible resistance.

# Capacitors in Series and in Parallel

- ◆ As with resistors, there are equivalent capacitance when multiple capacitors in series
- ◆ Capacitors in series all have the same amount of charge on each plate of the capacitor
- ◆ Capacitors in parallel are charged to the same voltage

$$C_p = \sum C_n$$
$$\frac{1}{C_s} = \sum \frac{1}{C_n}$$

# Summary of Equations

$$I = \frac{Vq}{Vt}$$

$$V = IR$$

$$R = \rho \frac{L}{A}$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

$$V = V_0 \sin 2\pi ft$$

$$I = I_0 \sin 2\pi ft$$

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$\bar{P} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

$$R_s = \sum R_n$$

$$\frac{1}{R_p} = \sum \frac{1}{R_n}$$

$$C_p = \sum C_n$$

$$\frac{1}{C_s} = \sum \frac{1}{C_n}$$